

**Ist semester 2017 – 18**  
**Computer science – II**

**Std: XI**

**Marks:50**

**Date:**

**Time:**

**Q.1.A) Select the correct alternative and rewrite the following:**

**4**

- 1) A rheostat is a \_\_\_\_\_ resister.  
a) variable b) linear c) fixed d) non - linear
- 2) For PTC thermistor the resistance value \_\_\_\_\_ with increase in temperature.  
a) Increases b) decreases c) equals d) none of these
- 3) In case of AND gate , if A is true and B is true then Y is \_\_\_\_\_.  
a) true b) false c) high d) low
- 4) NAND gate can be achieved by connecting a NOT gate to \_\_\_\_\_ gate.  
a) AND b) OR c) NAND d) NOR

**B) Answer any two of the following:**

**6**

- 1) Differentiate between active and passive components.
- 2) Explain AND gate.
- 3) Write a note on resistor. Give its types.

**Q.2.A) Answer any two of the following:**

**6**

- 1) Explain energy band diagrams for conductor, insulator and semiconductor.
- 2) Give significance of logic gates.
- 3) Explain a wire wound resistor with diagram.

**B) Answer any one of the following:**

**4**

- 1) Find the value of resistance for the following. Draw table for the same.  
Green, blue, orange silver
- 2) State and prove Demorgans theorem.(Any one)

**Q.3.A) Answer any two of the following: 6**

- 1) Explain RC time constant.
- 2) Draw a diagram for the following equation using logic gates.

$$Y = \overline{(A + B)} + (A.B)$$

- 3) Explain three types of inductors.

**B) Answer any one of the following: 4**

- 1) "NAND and NOR are called universal building blocks". Explain
- 2). Explain any two types of non-electrolytic capacitors.

**Q.4.A) Answer any two of the following: 6**

- 1) Differentiate between N type and P type semiconductors.
- 2) Write a short note on importance of ICs .
- 3) Explain EXOR gate.

**B) Answer any one of the following: 4**

- 1) Explain transformer. Explain its principle of working
- 2) Solve the given equation and draw logic diagram for the simplified form using logic gates.

$$(A+B)(A+C)$$

**Q.5.A) Answer any two of the following: 10**

- 1) What is a PN junction diode? Explain forward and reverse bias.
- 2) Explain decoder.
- 3) Explain 4:1 MUX.

**OR**

- 1) Explain full adder with diagram. Give its truth table and symbol.
- 2) Explain charging and discharging of capacitors with diagrams. Draw respective graphs
- .3) Explain Encoder with diagram.

